

R3 - Hardware Training 2

Ryan Padoco

7.4.2 Astable Operation

If the circuit is connected as shown in Figure 14 (pins 2 and 6 connected) it will trigger itself and free run as a multivibrator. The external capacitor charges through $R_A + R_B$ and discharges through R_B . Thus the duty cycle may be precisely set by the ratio of these two resistors.

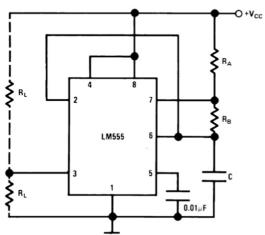


Figure 14. Astable


timer runs
on a V_{CC}
From 5V-15V
standard.

In this mode of operation, the capacitor charges and discharges between $1/3 V_{CC}$ and $2/3 V_{CC}$. As in the triggered mode, the charge and discharge times, and therefore the frequency are independent of the supply voltage.

We Want Astable Configuration for a
Constant clock pulse.

about
100x →

Device Functional Modes (continued)

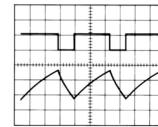

$V_{CC} = 5 \text{ V}$
TIME = 20 $\mu\text{s}/\text{DIV}$.
 $R_A = 3.5 \text{ k}\Omega$
 $R_B = 3 \text{ k}\Omega$
 $C = 0.01 \mu\text{F}$

Figure 15. Astable Waveforms

The charge time (output high) is given by:

$$t_1 = 0.693 (R_A + R_B) C$$

And the discharge time (output low):

$$t_2 = 0.693 R_B C$$

Thus the total period is:

$$T = t_1 + t_2 = 0.693 (R_A + 2R_B) C$$

The frequency of oscillation is:

$$f = \frac{1}{T} = \frac{1.44}{(R_A + 2R_B) C}$$

since R_A is negligible (1)

$$T = 1.386 R_B C \quad (2)$$

$$T = 1 \text{ s} \Rightarrow \frac{1}{C} = \frac{0.7215}{R_B} \quad (3)$$

$$T = 1 \text{ s} \Rightarrow \frac{1}{C} = \frac{0.7215}{R_B} \quad (4)$$

Figure 16 may be used for quick determination of these RC values.

The duty cycle is:

$$D = \frac{R_B}{R_A + 2R_B}$$

for 50% duty

$$R_A \ll R_B$$

$$\Rightarrow D \approx \frac{R_B}{2R_B} = 50\%$$

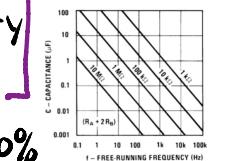


Figure 16. Free Running Frequency

↳ To make R_A negligible but still usable (Won't blow) we can make it $R_A = 1 \text{ k}\Omega$ with its counterpart $R_B = 100 \text{ k}\Omega$

This makes $D = 49.8\%$ Which is tolerable for this application

↳ Now that we have our duty matched, we need 1s uptime for the LED

→ high for 50% a period, so $T = 2\text{s}$ gives us this desired value

$$C \approx \frac{0.7215}{150 \text{ k}\Omega} = 4.81 \mu\text{F}$$


∴ this is not a commonly rated capacitor,
so we will use a $4.7 \mu\text{F}/6.3\text{V}$ electrolytic capacitor instead.

↳ This capacitor yields a

$$T = 0.693(1 \text{ k} + 300 \text{k})4.7 \mu\text{F} = 0.9804 \text{ s}$$

→ 0.49s on time

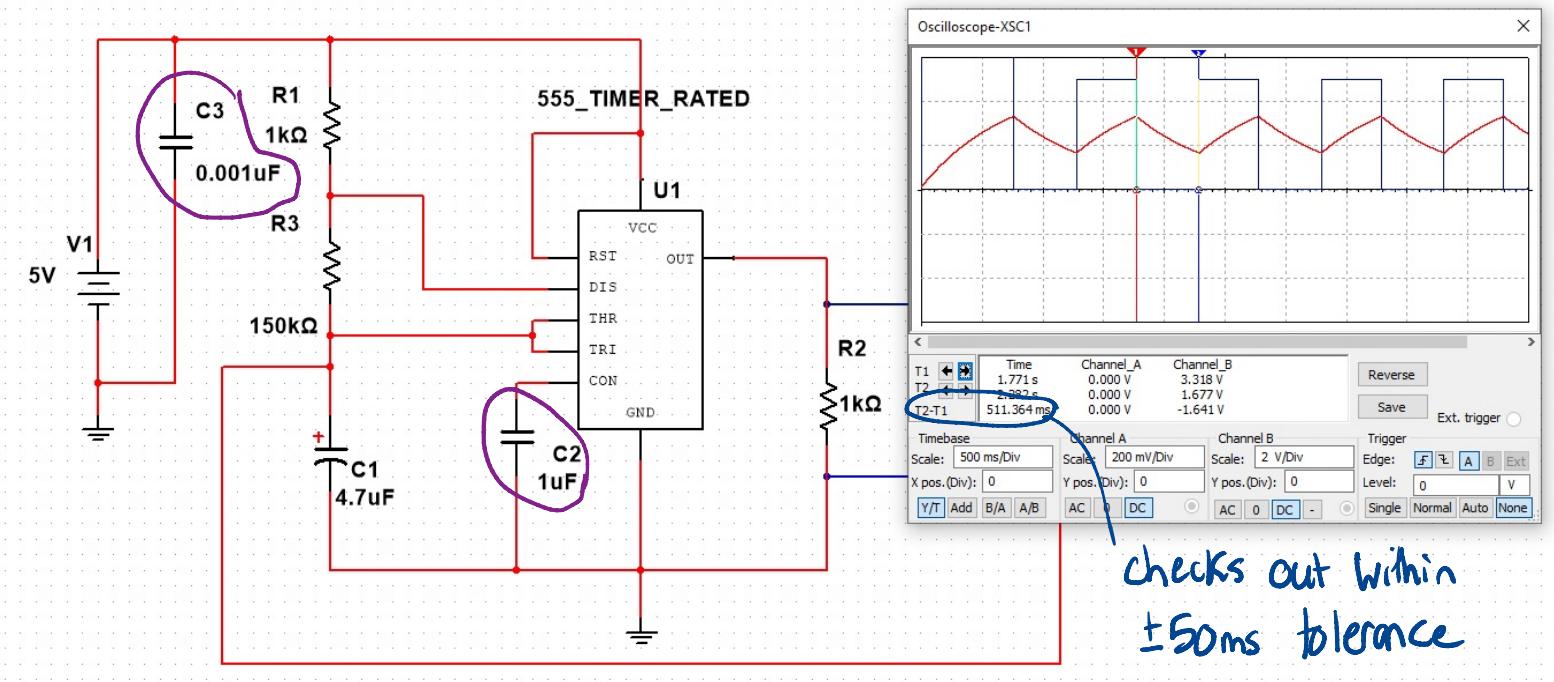↳ I verified these values on Multisim and everything worked, but was not consistent until I added C_2 & C_3 .



- C_2 minimizes the noise in the circuit (as depicted by datasheet)
 C_3 limits overpulling current from V_{cc} , more consistent

Dual channel FF has +7V max V_{cc} . Limit it to 5.0V!

